

Rubric:

A1:

Equation for QA or Q1: 1 mark

Equation for QB or Q2: 1 mark

Equation for z: 1 mark

State table: 2 marks

Sequence detection and explanation: 5 marks

A2:

QA: 1 mark

QB: 1 mark

QC: 3 marks.


## ECE111: Digital Circuits: End-Semester Exam

Date: Nov. 28, 2018
 
### Set A – 15 Marks


*Tasmine*

- A1. Derive the state table for the circuit given below. What sequence of input values on wire w is detected by this circuit?



10 Marks

 - A2. For the circuit given below, draw the timing diagram (for at least 10 clock cycles), starting with QA = QB = QC = 0. All FFs are JK FF and triggered on negative edge.



5 Marks

Please note that for set-B, all flip-flops should be D-type only.

Rubric for B1:

Circuit diagram: 4 marks

Explanation: 2 marks

Rubric for B2:

Mod10 counter design and circuit: 3 marks

Integration with B1: 1 mark

Rubric for B3:

state table: 2 marks

FF input expressions : 3 marks or circuit diagram: 3 marks

## Set B – 15 Marks

Sub hadip

- B1. A sequential circuit has two inputs,  $w_1$  and  $w_2$ , and an output,  $z$ . Its function is to compare the input sequences on the two inputs. If  $w_1 = w_2$  during any four consecutive clock cycles, the circuit produces  $z = 1$ ; otherwise,  $z = 0$ .

For example

$w_1$  : 0110111000110

$w_2$  : 1110101000111

$z$  : 0000100001110

6 Marks

- B2. Extend the circuit in B1 to count the number of times the output is 1. The count should be from 0 to 10. After 10, it resets to 0.

4 Marks

- B3. Design a *three-bit* counter like circuit controlled by the input  $w$ . If  $w = 1$ , then the counter adds 2 to its contents, wrapping around if the count reaches 8 or 9. Thus if the present state is 6 or 7, then the next state becomes 0 or 1, respectively. If  $w = 0$ , then the counter subtracts 1 from its contents, acting as a normal down-counter. Use D flip-flops in your circuit.

5 Marks

Rubric For C1:

Compute time period as 1ns or 1000 ps: 0.5 marks

Path from F1 to F3:

Setup Analysis:  $1000 > 10+50+30$ : No violation [0.5 mark]

Hold Analysis:  $10+50 > 20$ : No violation [0.5 Mark]

Path from F2 to F3:

Setup Analysis:  $1000 > 10+50+30$ : No violation [0.5 mark]

Hold Analysis:  $10+50 > 20$ : No violation [0.5 Mark]

Path from F1 to F2:


Setup Analysis:  $1000 > 10+30$ : No violation [0.5 mark]

Hold Analysis:  $10 > 20$ : Violated [2 Mark]

### Set C – 10 Marks

Vaibhav.

C1.

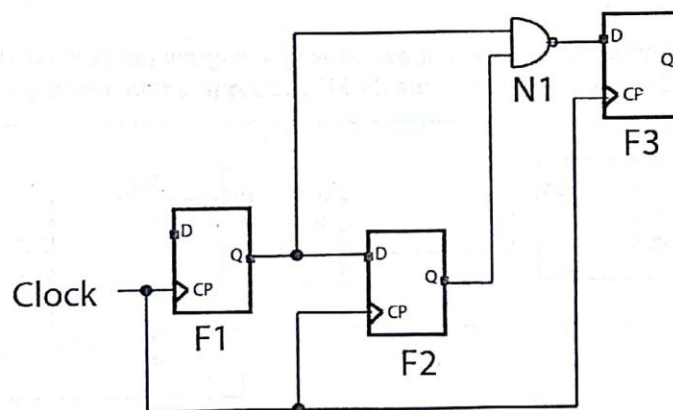

A sequential circuit is shown above. The following data is valid for all the flip-flops F1, F2 and F3:

Setup Time = 30 ps

Hold Time = 20 ps

Clock-to-Q Delay = 10 ps

The delay of the NAND gate N1 is 50 ps.

The frequency of "Clock" is 1 GHz.

Ignore the delay of all the wires.

Find if there is any timing problem in the above circuit.

5 Marks


## Rubric For C2:

Circuit 1: 0.5 Marks For Identifying that this is not a well-formed K-stage pipeline  
2 Marks for explanation (Two paths must be shown/described that have different number of registers in the path)


Circuit 2: 0.5 Marks For Identifying that this is a well-formed K-stage pipeline  
1 Mark for explanation that all paths have same number of registers  
1 Mark for identifying that  $K=3$  or  $K=4$

C2. In the following two circuits, the combinational elements are shown as unshaded rectangles with non-zero propagation delay and the flip-flops are shown as fully-shaded black rectangles. For each of the two circuit state whether they represent well-formed K-stage pipeline. If a circuit represent a well-formed k-stage pipeline then find the value of K If a circuit does not represent a well-formed k-stage pipeline then explain the reason for it.

### 1. Circuit-1

 

### 2. Circuit 2

 

5 Marks