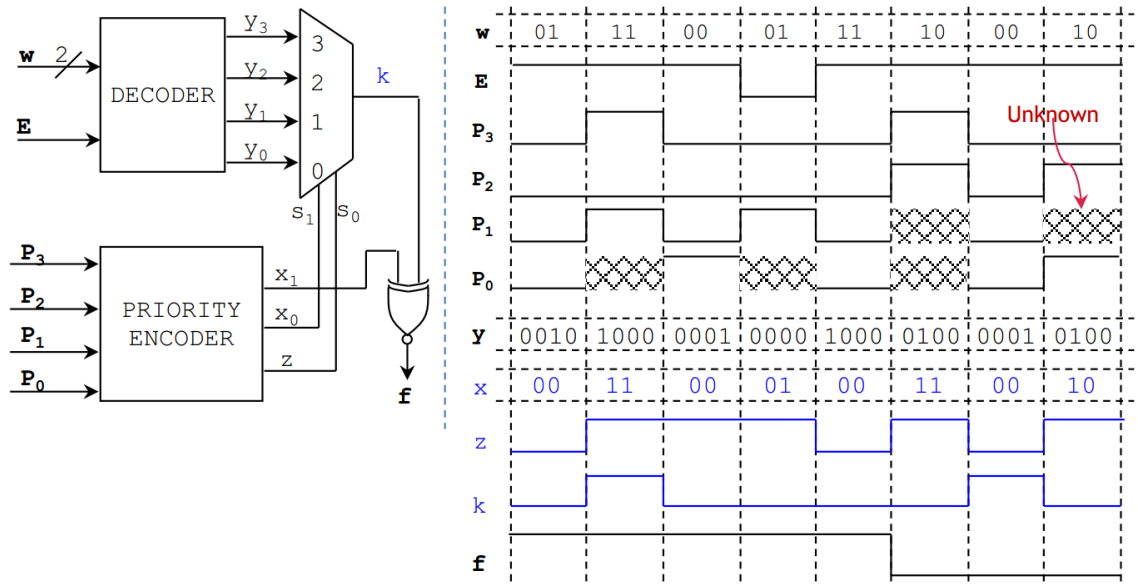



Digital Circuits Quiz-2 (3rd October, 2018)

Time: 30 minutes

1. Complete the timing diagram of the circuit shown below. The output z of the priority encoder is the valid bit indicator. The signal x and y is to be represented compactly as x_1x_0 and $y_3y_2y_1y_0$, respectively. **[5 Marks]**



2. Consider the circuit shown below where the output of a 3-bit adder needs to be displayed on the two digits of the 7-segment display. For example, if the adder output is 9, then circuit should display 09 where 0 should be displayed on left display and 9 on right display. Existing BCD-to-7 segment decoder works only when input number is between 0 and 9 and we have to use it since it has been hardwired to 7-segment display board. You need to design combinational circuit between Adder and 7-segment decoder (shown as question mark in the Figure below) so that the adder output is correctly displayed on the 7-segment display. **[5 Marks]**

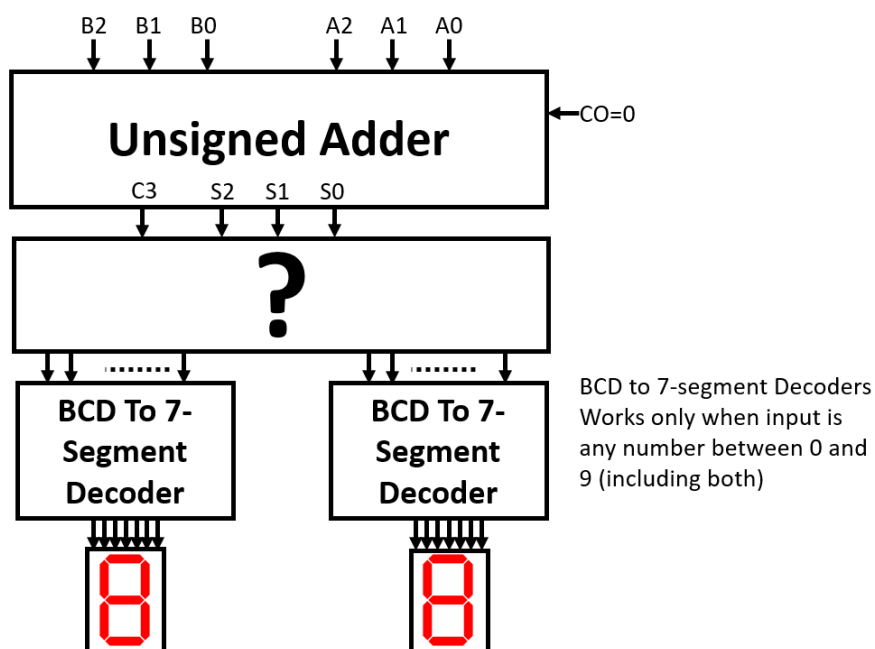

Approach 1:

Soln 2.

O/P of Unsigned Adder is i/P to the Question mark Block. According to the input we have to

differentiate the o/p

eg: $14 - \begin{matrix} C_3 & S_2 & S_1 & S_0 \\ 1 & 1 & 1 & 0 \end{matrix} \rightarrow \begin{matrix} X_3 & X_2 & X_1 & X_0 \\ 0 & 0 & 0 & 1 \end{matrix} \quad \begin{matrix} Y_3 & Y_2 & Y_1 & Y_0 \\ 0 & 1 & 0 & 0 \end{matrix}$

More over, Addition can never be ⁽¹⁾15. ⁽⁴⁾Take don't care. Similarly for all combinations.

C_3	S_2	S_1	S_0	X_3	X_2	X_1	X_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0				0	0	0	0	0
0	0	0	1				0	0	0	0	1
0	0	1	0				0	0	0	1	0
0	0	1	1				0	0	0	1	1
0	1	0	0				0	0	1	0	0
0	1	0	1				0	0	1	0	1
0	1	1	0				0	0	1	1	0
0	1	1	1				0	0	1	1	1
1	0	0	0				0	1	0	0	0
1	0	0	1				0	1	0	0	1
1	0	1	0				1	0	0	0	0
1	0	1	1				1	0	0	0	1
1	1	0	0				1	0	0	1	0
1	1	0	1				1	0	0	1	1
1	1	1	0				1	0	1	0	0
1	1	1	1				1	0	1	0	1
							X	X	X	X	X

↑
↓
are zero

K-map for

X_0

$C_3 \backslash S_2 S_1 S_0$	00	01	11	10
00				
01				
11	1	1	1	1
10			1	1

$$X_0 = C_3 S_2 + C_3 S_1$$

$C_3 \backslash S_2 S_1 S_0$	00	01	11	10
00				
01				
11			X	
10	1	1		

$$Y_3 = C_3 \bar{S}_2 \bar{S}_1$$

$C_3 \backslash S_2 S_1 S_0$	00	01	11	10
00		1	1	
01		1	1	
11		1	X	
10		1	1	

$$Y_0 = S_0$$

$$Y_2 = \bar{C}_3 S_2 + S_2 S_1$$

$$Y_1 = \bar{C}_3 S_1$$

Draw circuit Accordingly.

Approach 2:

Question can also be solved by using Binary Adder approach.

eg: $14 \rightarrow 1110$ is '>'g'


\therefore Add '6'

$$\begin{array}{r} 1110 \\ + 0110 \\ \hline 110100 \\ 00010100 \\ \hline 1 \quad 4 \end{array}$$

$\therefore C_3 S_2 S_1 S_0$
0000
0
Don't nothing

1000	0
1010	1
1011	1
1100	1
1101	1
1110	1
1111	1

Add '+6'

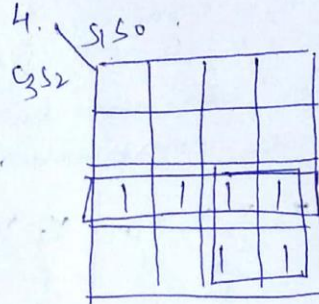

$$O/P = C_3 S_2 + S_1 C_3$$

