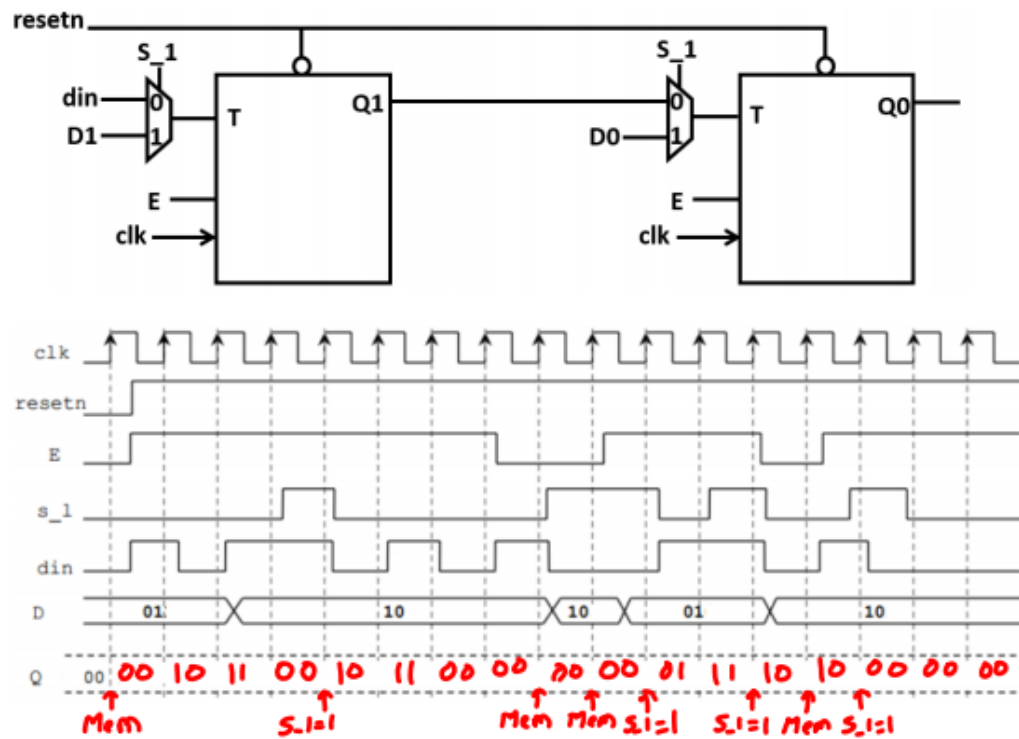


Digital Circuits Quiz-3 (29th October, 2018)

Time: 40 minutes

- Consider the following circuit consisting of two T-FFs (toggle Flip-flops) with memory (when $T=0$) and toggle (when $T=1$) states. When $E=0$, T-FFs goes into memory state irrespective of value of input T . Complete the timing diagram where $D=\{D1,D0\}$ and $Q=\{Q1,Q0\}$.



2(a)

$$Q1(t+1) = Q2(t) \oplus Q3(t)$$

$$Q2(t+1) = Q1(t)$$

$$Q3(t+1) = Q2(t)$$

2(b)

$$S(1) = \{1, 0, 0\}$$

$$S(2) = \{0, 1, 0\}$$

$$S(3) = \{1, 0, 1\}$$

$$S(4) = \{1, 1, 0\}$$

$$S(5) = \{1, 1, 1\}$$

$$S(6) = \{0, 1, 1\}$$

$$S(7) = \{0, 0, 1\}$$

$$S(8) = \{1, 0, 0\}$$

....

Repetition occurs such that $S(0) = S(7)$, $S(1) = S(8)$ and so on.

The output at clock cycle t is same as $t\%7$ (*modulus of 7*).

$$S(100) = S(100\%7) = S(2) = \{0, 1, 0\}$$

$$S(1000) = S(1000\%7) = S(6) = \{0, 1, 1\}$$